

# LEDs



[Testing](#) | [Colour](#) | [Sizes & shapes](#) | [Resistor](#) | [LEDs in series](#) | [LED data](#) | [Flashing](#) | [Displays](#)



Also see: [Lamps](#) | [Diodes](#)

## LED = Light Emitting Diode

LEDs emit light when an electric current passes through them.

The electrical behaviour of an LED is quite different from a lamp and it must be protected from passing excessive current, usually this is achieved by connecting a resistor in series with the LED. **Never connect an LED directly to a battery or power supply.**

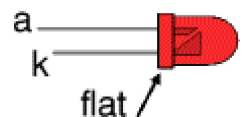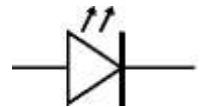LEDs must be connected the correct way round, the diagram may be labelled **a** or **+** for anode and **k** or **-** for cathode (yes, it really is k, not c, for cathode). The cathode is the short lead and there may be a slight flat on the body of round LEDs. If you can see inside the LED the cathode is the larger electrode but this is not an official identification method.



## Soldering LEDs

LEDs can be damaged by heat when soldering but the risk is small unless you are very slow. No special precautions are needed for soldering most LEDs.


Rapid Electronics: [LEDs](#)

## Testing an LED

**Never connect an LED directly to a battery or power supply** because the LED is likely to be destroyed by excessive current passing through it.

LEDs must have a resistor in series to limit the current to a safe value, for testing purposes a  $1k\Omega$  resistor is suitable for most LEDs if your supply voltage is 12V or less. **Remember to connect the LED the correct way round.**

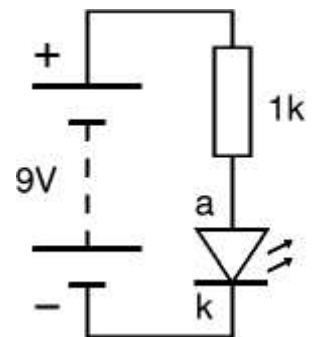
Please see below for an explanation of how to work out a suitable [resistor](#) value for an LED.


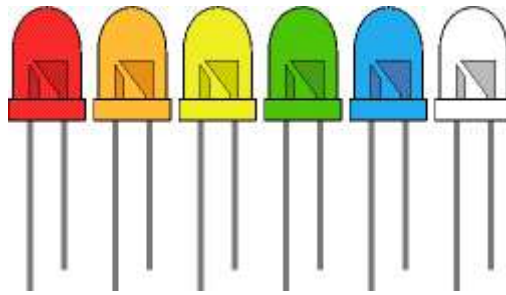
## LED Colours

The colour of an LED is determined by its semiconductor material, not by the colouring of the 'package' (the plastic body). LEDs of all colours are available in uncoloured packages which may be diffused (milky) or clear (often described as 'water clear'). The coloured packages are also available as diffused (the standard type) or transparent.

Blue and white LEDs may be more expensive than the other colours.



## Bi-colour LEDs


A bi-colour LED has two LEDs wired in 'inverse parallel' (one forwards, one backwards) combined in one package with two leads. Only one of the LEDs can be lit at one time and they are less useful than the tri-colour and RGB LEDs described below.

## Tri-colour LEDs

The most popular type of tri-colour LED has a red and a green LED combined in one package with three leads. They are called tri-colour because mixed red and green light appears to be yellow and this is produced when both the red and green LEDs are on.

The diagram shows the construction of a tri-colour LED. Note the different lengths of the three leads. The centre lead (k) is the common cathode for both LEDs, the outer leads (a1 and a2) are the anodes to the LEDs allowing each one to be lit separately, or both together to give the third colour.

Rapid Electronics: [red/green LED](#)

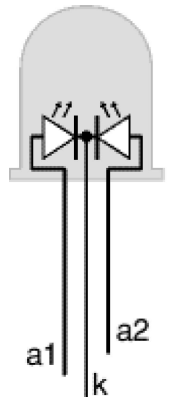

## RGB LEDs

RGB LEDs contain Red, Green and Blue LEDs in one package. Each internal LED can be switched on and off separately allowing a range of colours to be produced:

- **Red** + **Green** gives Yellow
- **Red** + **Blue** gives Magenta
- **Green** + **Blue** gives Cyan
- **Red** + **Green** + **Blue** gives White

A wider range of colours can be produced by varying the brightness of each internal LED.

Rapid Electronics: [RGB LED](#)

## Sizes, Shapes and Viewing angles of LEDs

LEDs are available in a wide variety of sizes and shapes. The 'standard' LED has a round cross-section of 5mm diameter and this is probably the best type for general use, but 3mm round LEDs are also popular.

Round cross-section LEDs are frequently used and they are very easy to install on boxes by drilling a hole of the LED diameter, adding a spot of glue will help to hold the LED if necessary. LED clips (illustrated) are also available to secure LEDs in holes. Other cross-section shapes include square, rectangular and triangular.

Photograph © [Rapid Electronics](#)



As well as a variety of colours, sizes and shapes, LEDs also vary in their viewing angle. This tells you how much the beam of light spreads out. Standard LEDs have a viewing angle of 60° but others have a narrow beam of 30° or less.

[Rapid Electronics](#) stock a particularly wide selection of LEDs and their website is a good guide to the extensive range available including the latest high power LEDs.

## Calculating an LED resistor value

An LED must have a resistor connected in series to limit the current through the LED, otherwise it will burn out almost instantly.

The resistor value, R is given by:


$$R = (V_S - V_L) / I$$

R = resistor value in ohms ( $\Omega$ ).

$V_S$  = supply voltage.

$V_L$  = LED voltage (2V, or 4V for blue and white LEDs).

I = LED current in amps (A)

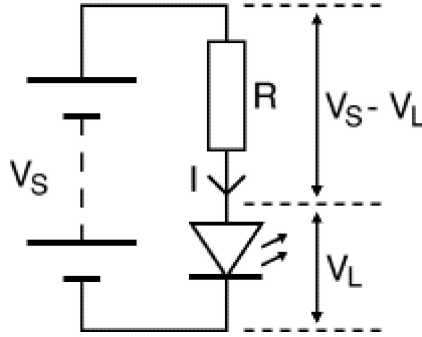

The LED current must be less than the maximum permitted for your LED. For standard 5mm diameter LEDs the maximum current is usually 20mA, so 10mA or 15mA are suitable values for many circuits. The current must be in amps (A) for the calculation, to convert from mA to A divide the current in mA by 1000.

If the calculated value is not available choose the nearest standard resistor value which is **greater**, so that the current will be a little less than you chose. In fact you may wish to choose a greater resistor value to reduce the current (to increase battery life for example) but this will make the LED less bright.

### For example

If the supply voltage  $V_S = 9V$ , and you have a red LED ( $V_L = 2V$ ), requiring a current  $I = 20mA = 0.020A$ ,  
 $R = (9V - 2V) / 0.02A = 350\Omega$ , so choose  $390\Omega$  (the nearest standard value which is greater).

### LED voltage

The LED voltage  $V_L$  is determined by the **colour** of the LED. Red LEDs have the lowest voltage, yellow and green are a little higher. Blue and white LEDs have the highest voltages.

For most purposes the exact value is not critical and you can use 2V for red, yellow and green, or 4V for blue and white LEDs.

### Working out the LED resistor formula using Ohm's law

Ohm's law says that the resistance of the resistor,  $R = V/I$ , where:

V = voltage across the resistor (=  $V_S - V_L$  in this case)

I = the current through the resistor


So  $R = (V_S - V_L) / I$

For more information on the calculations please see the [Ohm's Law](#) page.
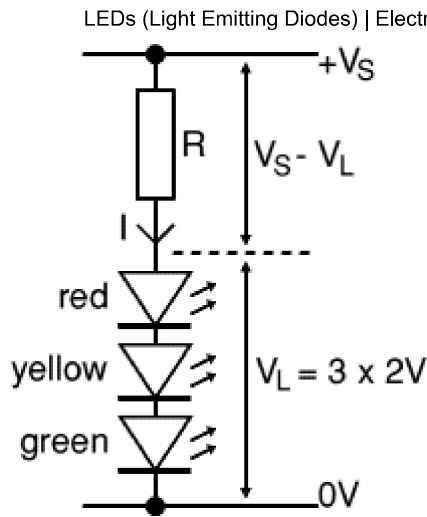
## Connecting LEDs in series

If you wish to have several LEDs on at the same time it may be possible to connect them in series. This prolongs battery life by lighting several LEDs with the same current as just one LED.

All the LEDs connected in series pass the **same current** so it is best if they are all the same type. The power supply must have sufficient voltage to provide about 2V for each LED (4V for blue and white) plus at least another 2V for the resistor. To work out a value for the resistor you must add up all the LED voltages and use this for  $V_L$ .



### Example calculations:

A red, a yellow and a green LED in series need a supply voltage of at least  $3 \times 2V + 2V = 8V$ , so a **9V battery** would be ideal.

$V_L = 2V + 2V + 2V = 6V$  (the three LED voltages added up).

If the supply voltage  $V_S$  is 9V and the current  $I$  must be  $15mA = 0.015A$ ,

Resistor  $R = (V_S - V_L) / I = (9 - 6) / 0.015 = 3 / 0.015 = 200\Omega$ ,


so choose  $R = 220\Omega$  (the nearest standard value which is greater).

## Avoid connecting LEDs in parallel!

Connecting several LEDs in parallel with just one resistor shared between them is generally a bad idea.

If the LEDs require slightly different voltages only the lowest voltage LED will light and it may be destroyed by the larger current flowing through it. Although identical LEDs can be successfully connected in parallel with one resistor this rarely offers any useful benefit because resistors are very cheap and the current used is the same as connecting the LEDs individually.

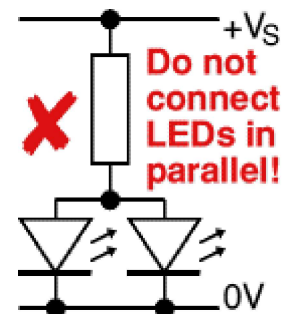**If LEDs are in parallel each one should have its own resistor.**



## Reading a table of technical data for LEDs

Suppliers' websites and catalogues usually provide tables of technical data for components such as LEDs. These tables contain a good deal of useful information in a compact form but they can be difficult to understand if you are not familiar with the abbreviations used. These are the important properties for LEDs:

- **Maximum forward current,  $I_F \text{ max}$ .**  
'Forward' just means with the LED connected correctly.
- **Typical forward voltage,  $V_F \text{ typ}$ .**  
This is  $V_L$  in the LED resistor calculation, about 2V, or 4V for blue and white LEDs.
- **Luminous intensity**  
Brightness at the specified current, e.g. 32mcd @ 10mA (mcd = millicandela).
- **Viewing angle**  
60° for standard LEDs, others emit a narrower beam of about 30°.
- **Wavelength**  
The peak wavelength of light emitted, it determines the colour of the LED, e.g. red 660nm, blue 430nm (nm = nanometre).

The following two properties can be ignored for most circuits:

- **Maximum forward voltage,  $V_F \text{ max}$ .**  
This can be ignored if you have a suitable resistor in series.

- **Maximum reverse voltage,  $V_R$  max.**

This can be ignored for LEDs connected the correct way round.


## Flashing LEDs

Flashing LEDs look like ordinary LEDs but they contain an [IC](#) (integrated circuit) as well as the LED itself. The IC flashes the LED at a low frequency, for example 3Hz (3 flashes per second). Flashing LEDs are designed to be connected directly to a particular supply voltage such as 5V or 12V without a series resistor. Check with the supplier to find the safe supply voltage range for a particular flashing LED. The flash frequency is fixed so their use is limited and you may prefer to build your own circuit to flash an ordinary LED, for example the [Flashing LED](#) project which uses a [555 astable](#) circuit.

Rapid Electronics: [flashing LEDs](#)
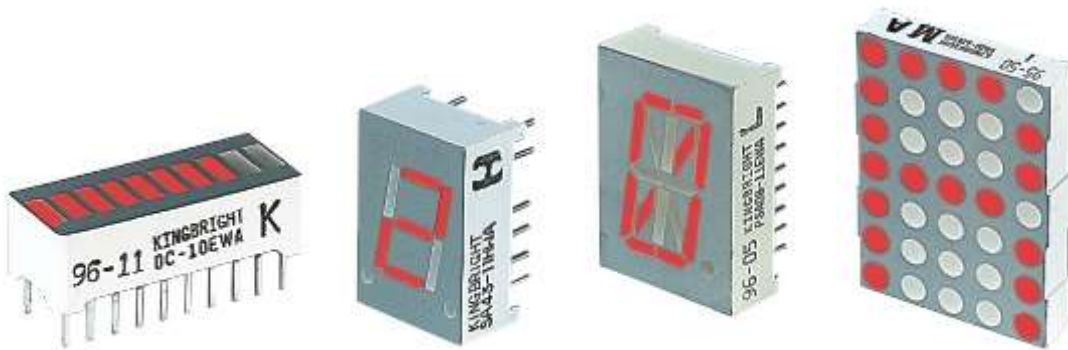
## LED Displays

LED displays are packages of many LEDs arranged in a pattern, the most familiar pattern being the 7-segment displays for showing numbers (digits 0-9). The pictures below illustrate some of the popular designs.



Bargraph, 7-segment, Starburst and Dot-matrix LED displays


Photographs © [Rapid Electronics](#)

Rapid Electronics: [LED displays](#)

### Pin connections of LED displays

There are many types of LED display and a supplier's catalogue or website should be consulted for the pin connections. The diagram on the right shows an example from [Rapid Electronics](#). Like many 7-segment displays, this example is available in two versions: Common Anode (SA) with all the LED anodes connected together and Common Cathode (SC) with all the cathodes connected together. Letters a-g refer to the 7 segments, A/C is the common anode or cathode as appropriate (on 2 pins). Note that some pins are not present (NP) but their position is still numbered.

Also see: [Display Drivers](#).

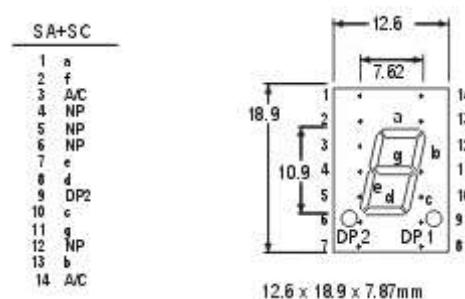

Pin connections diagram

© [Rapid Electronics](#)

[Rapid Electronics](#) have kindly allowed me to use their images on this website and I am very grateful for their support. They stock a wide range of LEDs, other components and tools for electronics and I am happy to recommend them as a supplier.

## Books on components:

- [Electronic Components, Volume 1](#)
  - [Electronic Components, Volume 2](#)
  - [Electronic Components, Volume 3](#)
- 

electronicsclub.info © John Hewes 2021